

# Multiplication

**1101**

**multiplicand**

x **0101**

**multiplier**

---

**1101**

**0000**

**1101**

**0000**

---

**1000001**

# Multiplication

**1101** multiplicand

Shift by 0

**1101**

**1**

multiplier

Shift by 1

~~1101~~0

**0**

Include term

Shift by 2

**1101**00

**1**

Shift by 3

~~1101~~000

**0**

MSB

**1000001**

# Multiplication

multiplicand

1101

RUNNING PRODUCT

00000000

1 + 1101 = 00001101

0 + 00000 = 00001101

1 + 110100 = 1000001


0 + 0000000 = 01000001

multiplier


# Algorithm

```
prod = 0
N = 32
while (N > 0)
{
    if (Mier & 1) prod += Mand;
    Mier >>= 1;
    Mand <<= 1;
    N--;
}
```


# Multiplier: Take #1

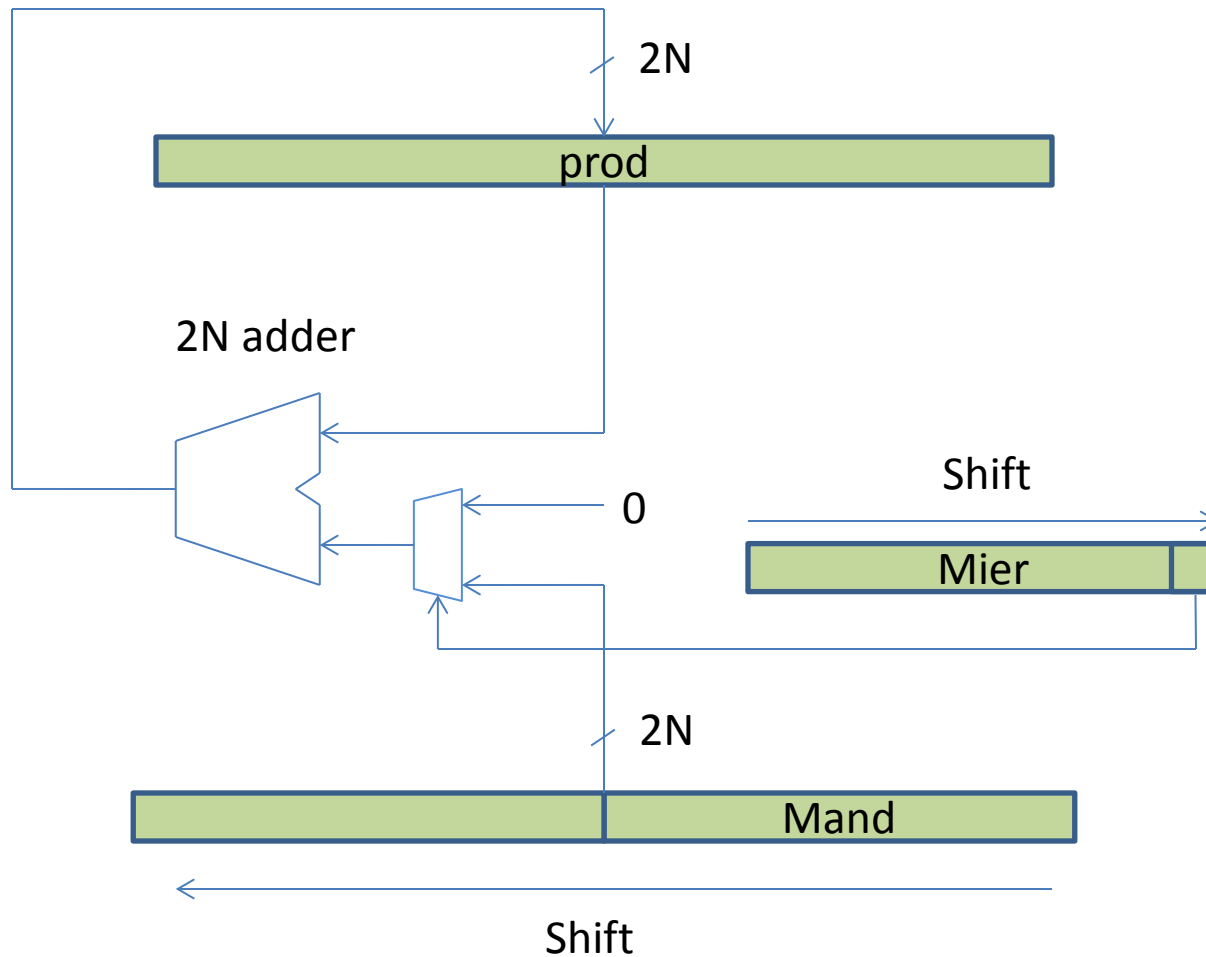


# Multiplier: Take #2

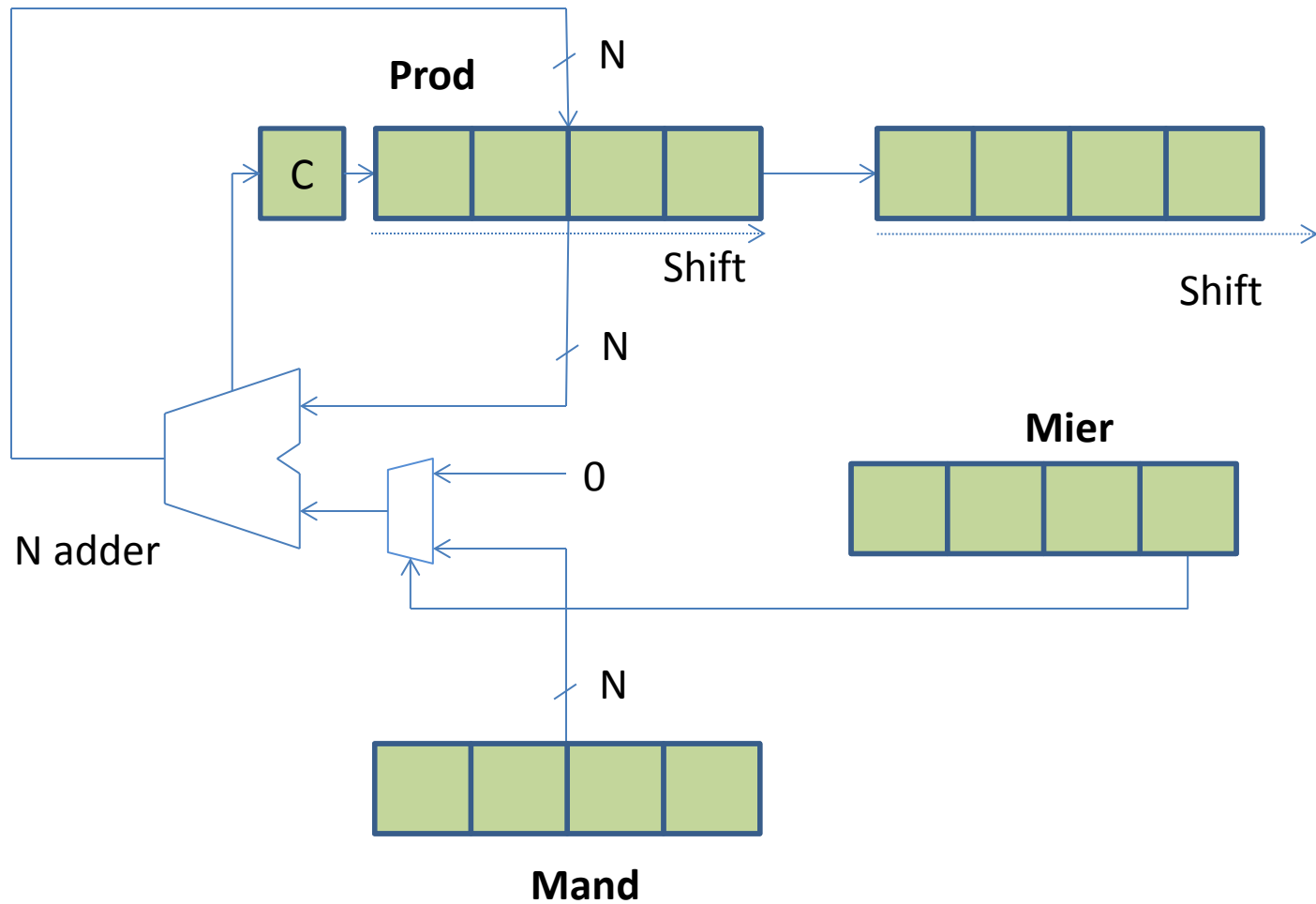

# Multiplier: Initial State

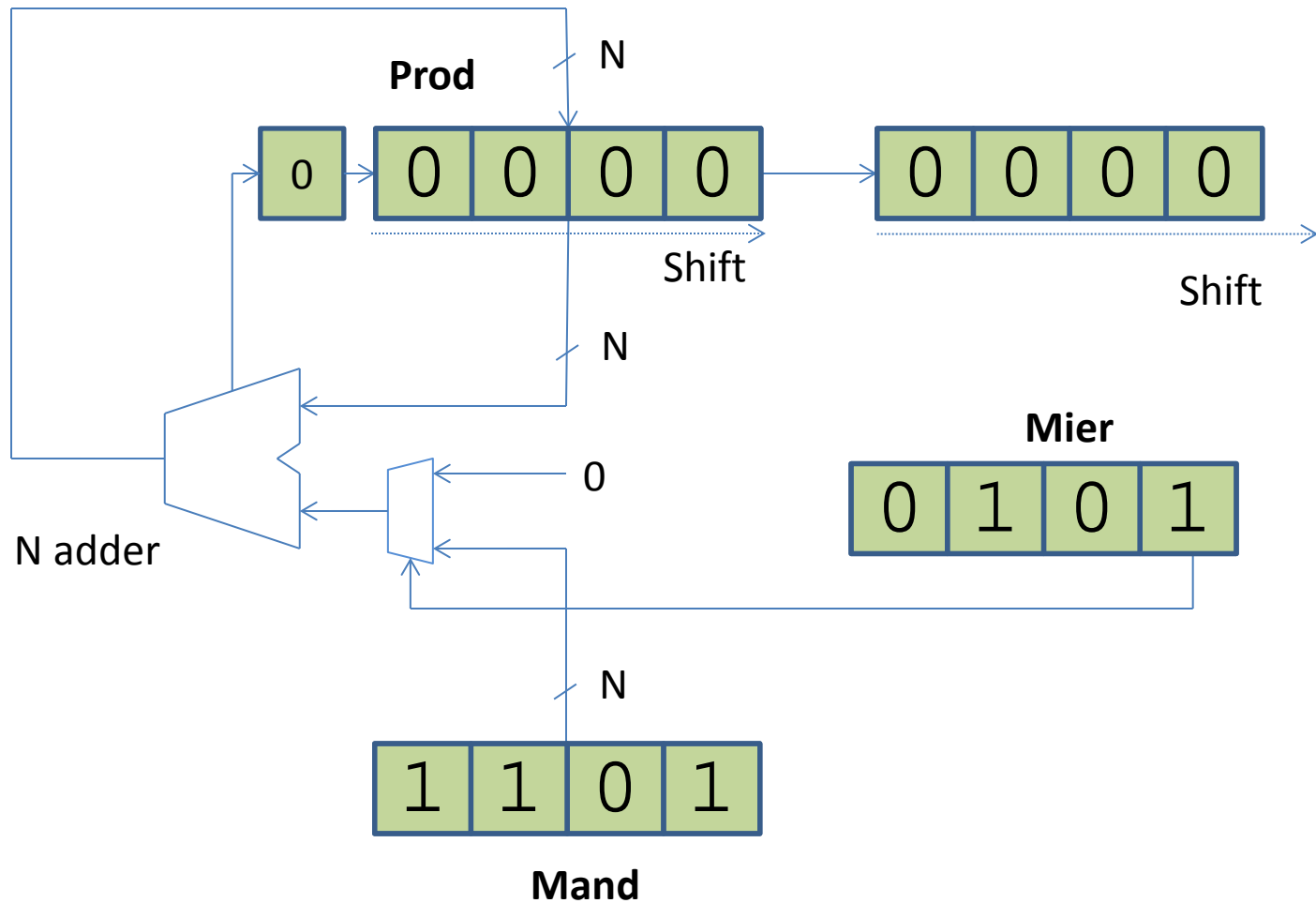


# Step 1: Add Mand to Prod

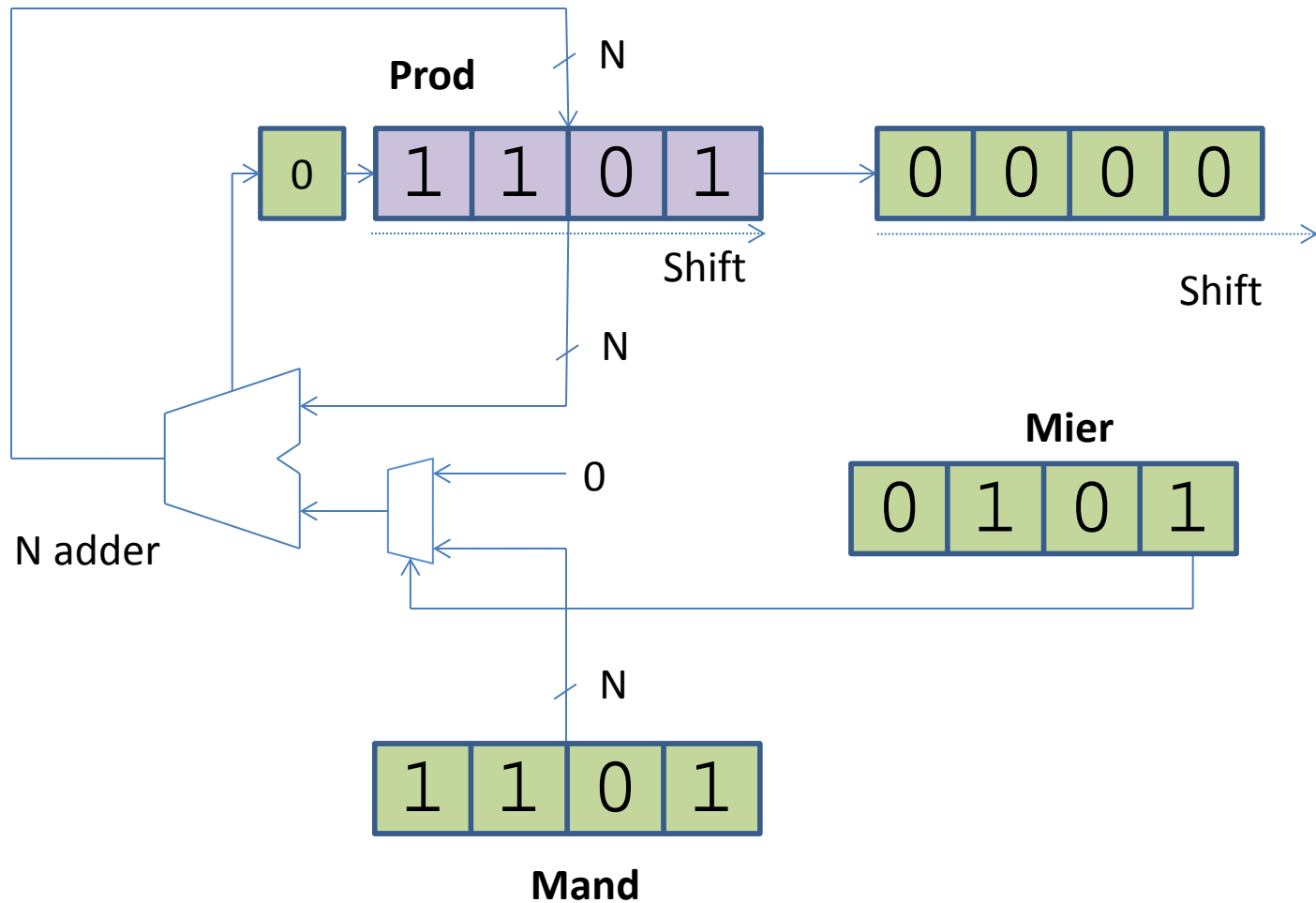





# Step 1: Shift Prod and Mier

 


# Step 2: Add Mand to Prod

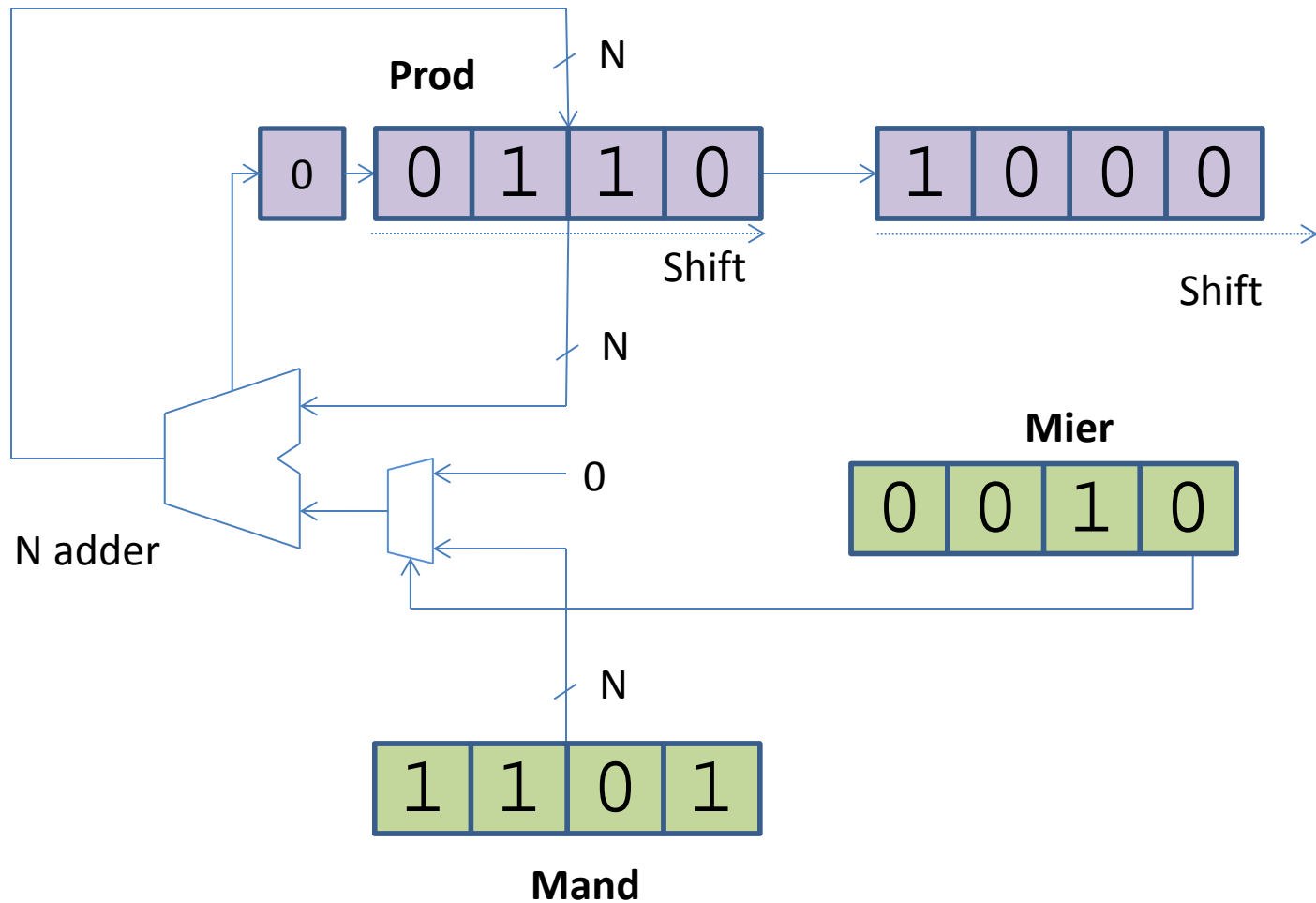


# Step 2: Shift Prod and Mier

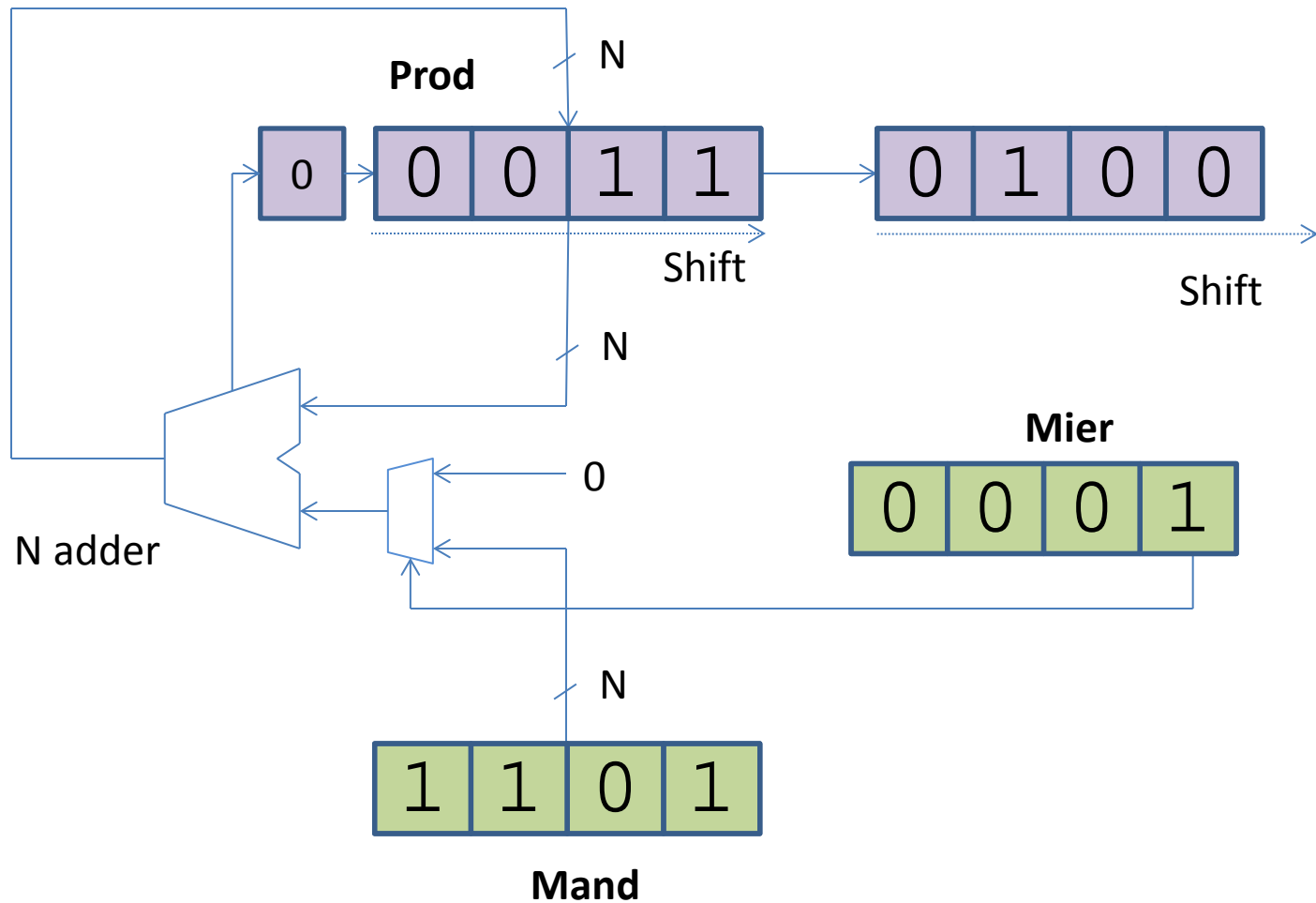


# Step 3: Add Mand to Prod

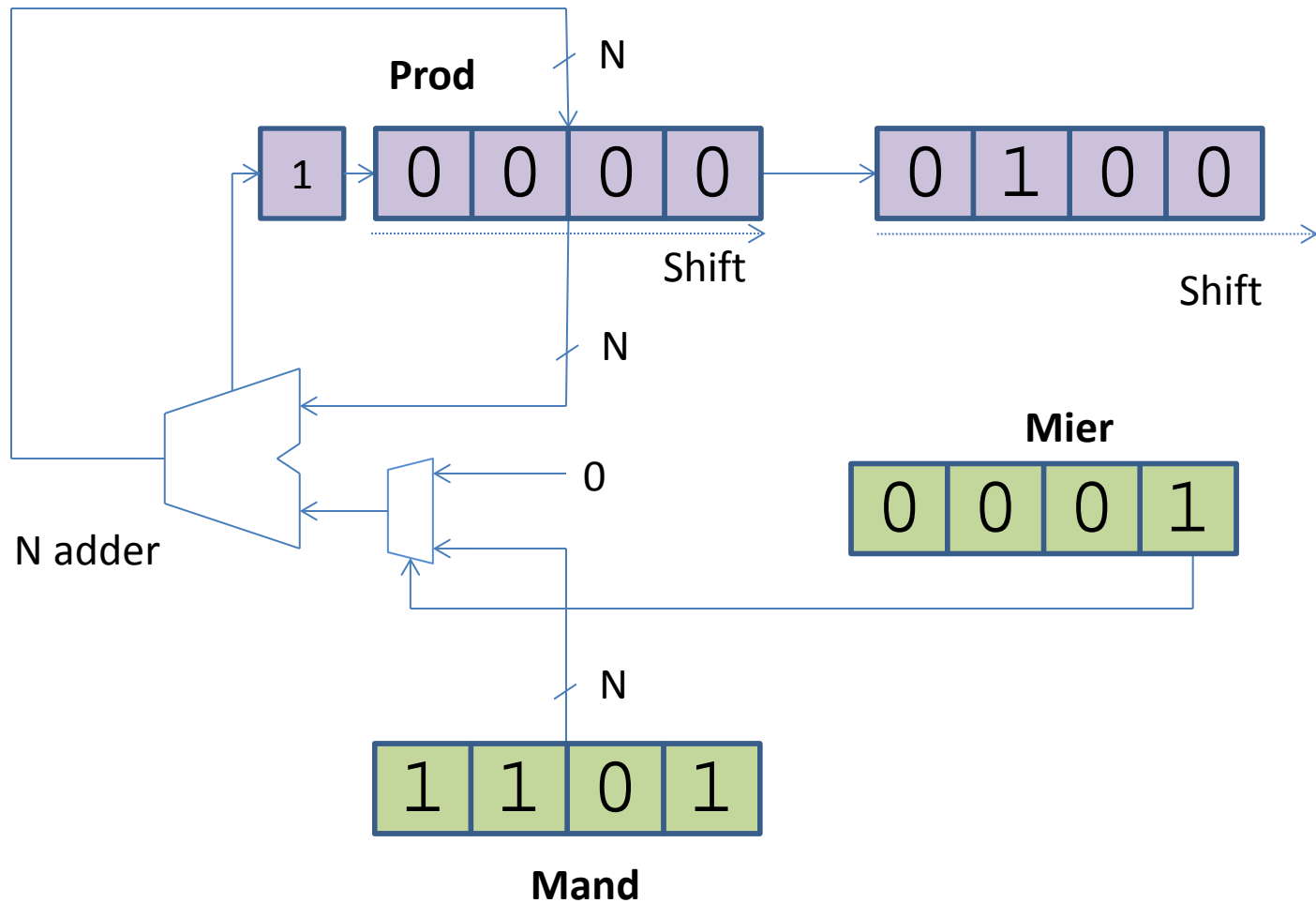


# Step 3: Shift Prod and Mier

 

# Step 4: Add Mand to Prod

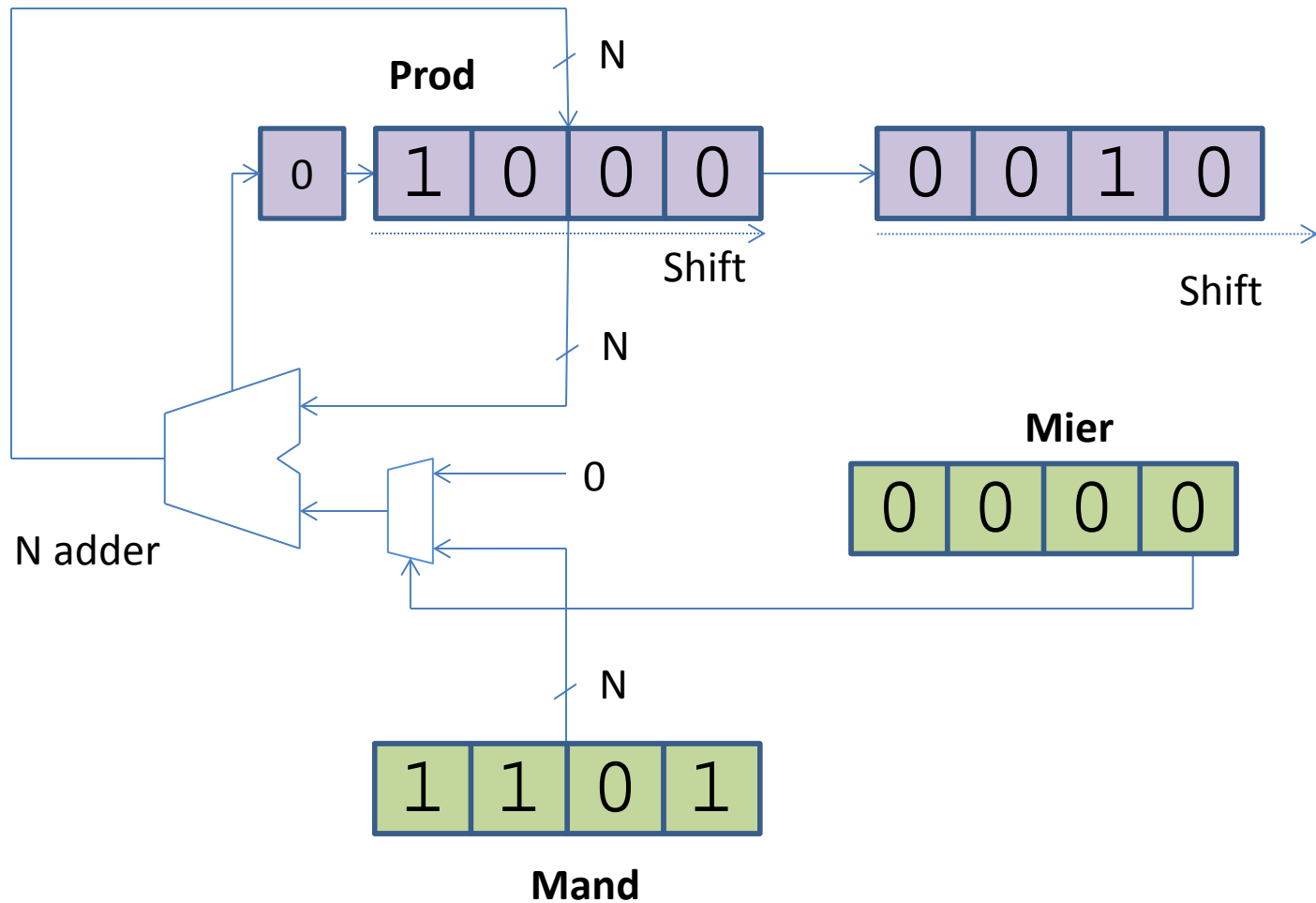

# Step 4: Shift Prod and Mier

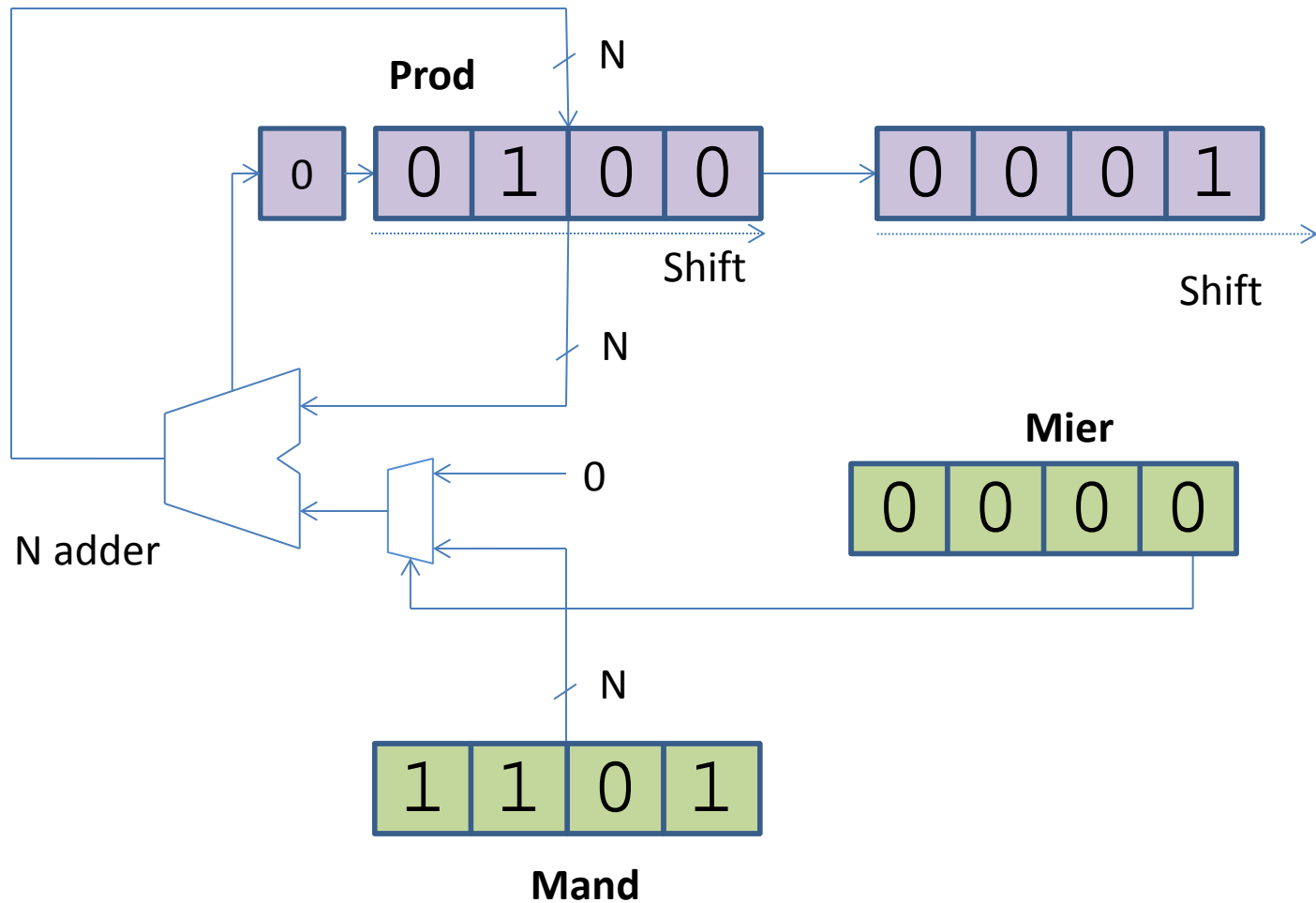


# Multiplier Take #2: How it works


Iteration	Step	Carry	Prod	Mier
0	Initial Value	0	0000 0000	0101
1	Add + Mult	0	1101 0000	0101
	Shift	0	0110 1000	0010
2	Add+Mult	0	0110 1000	0010
	Shift	0	0011 0100	0001
3	Add+Mult	1	0000 0100	0001
	Shift	0	1000 0010	0000
4	Add+Mult	0	1000 0010	0000
	Shift	0	0100 0001	0000



# Low Prod and Mier can be merged

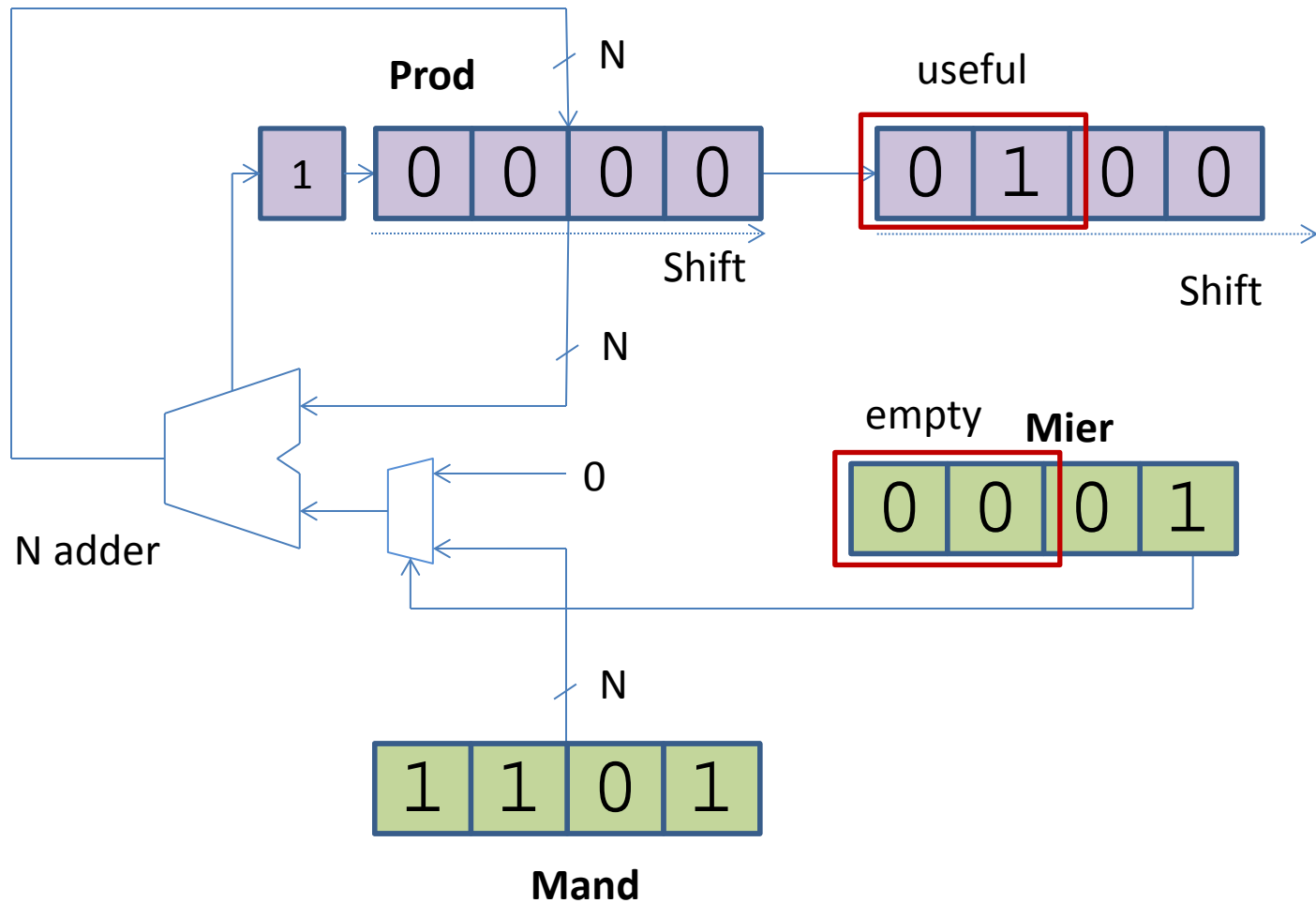

# Multiplier: Take #2

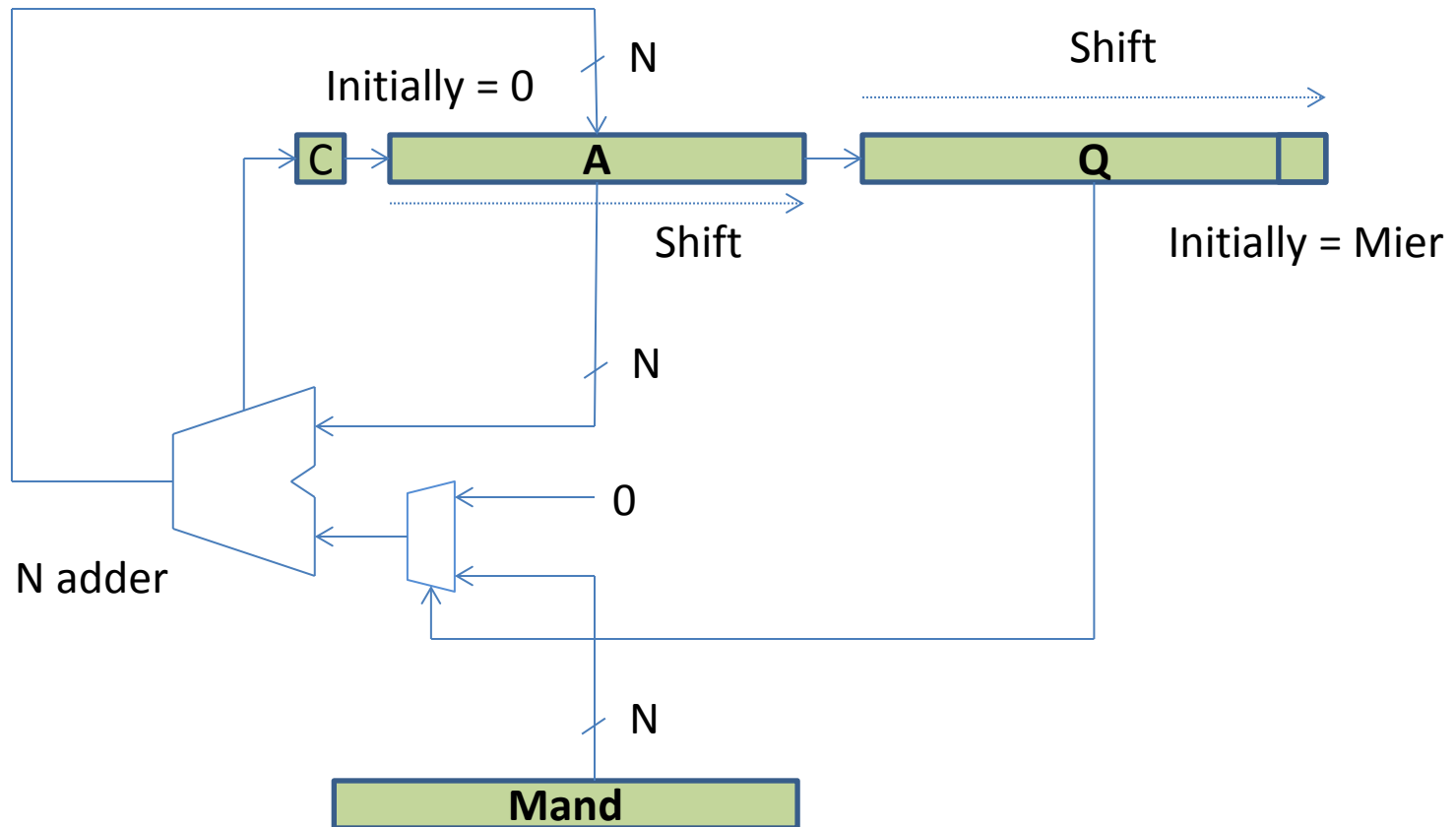

# Multiplier Array

1101 multiplicand

---

1101 1 multiplier

~~11010~~ 0

110100 1


~~1101000~~ 0

1000001



Include term


MSB

# Multiplier Array

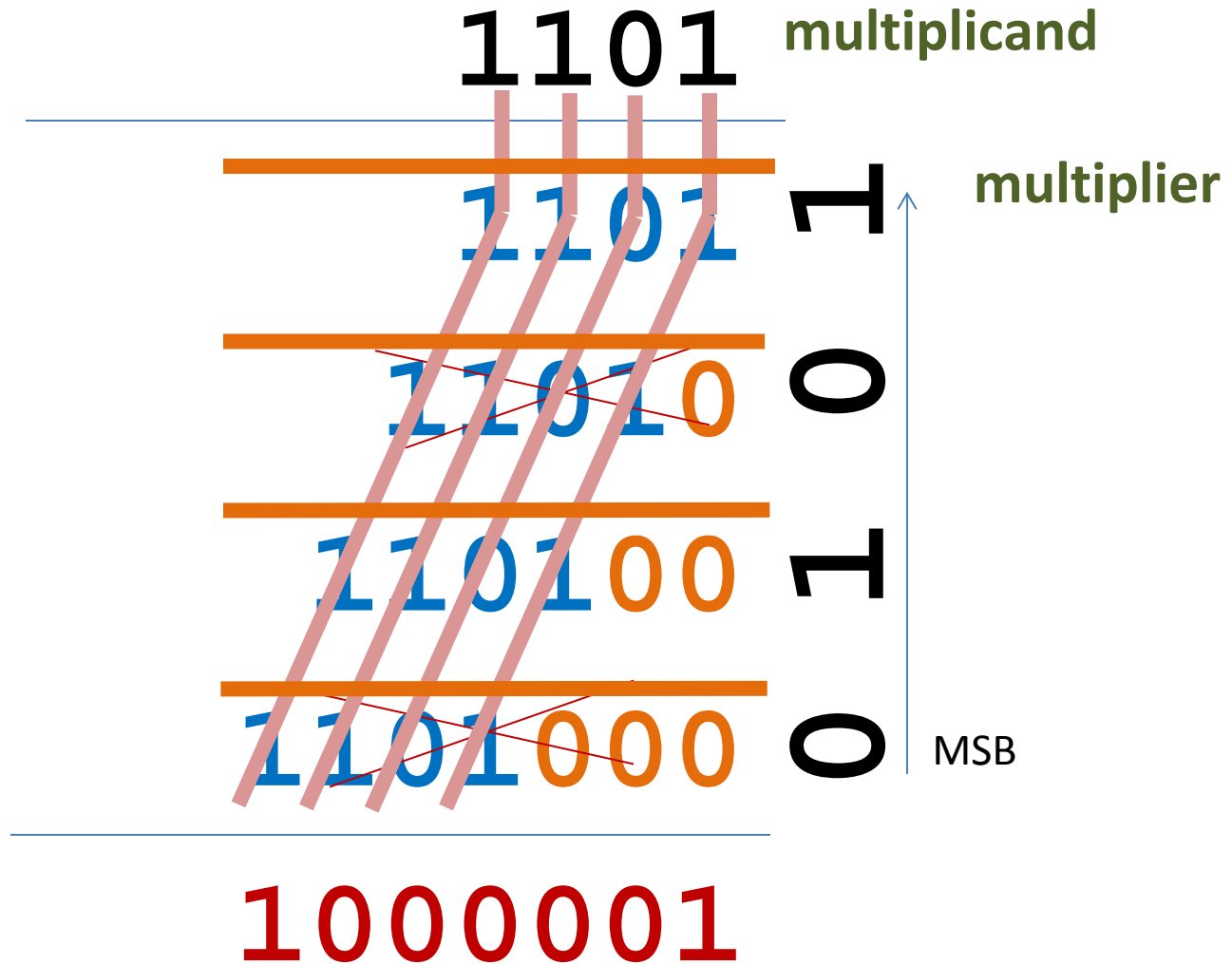


# Multiplier Array

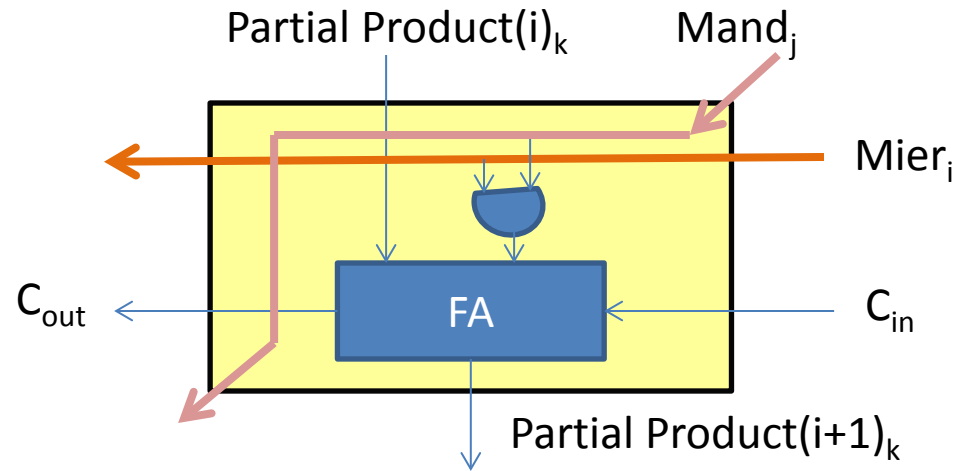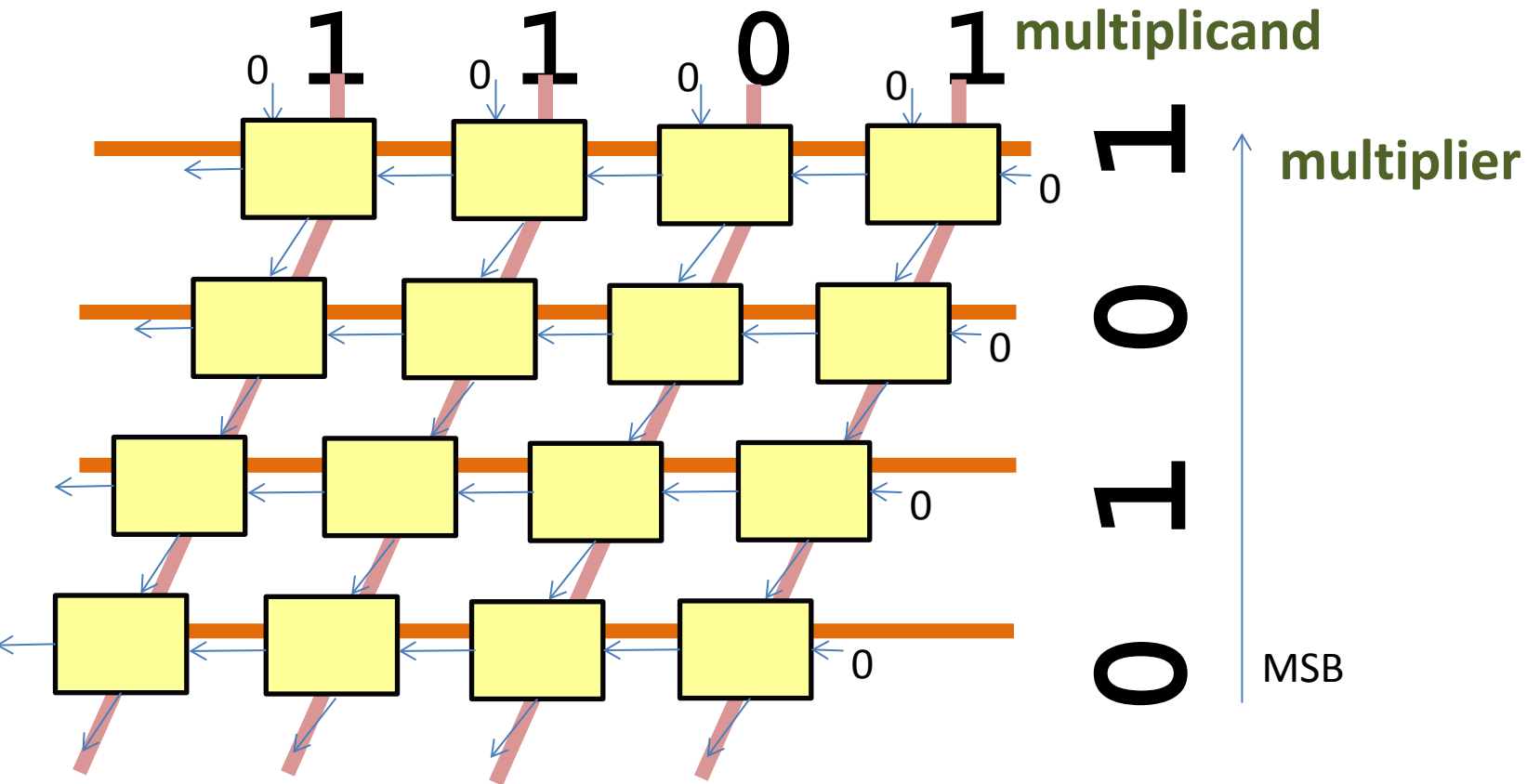


 

# Multiplier Array Example

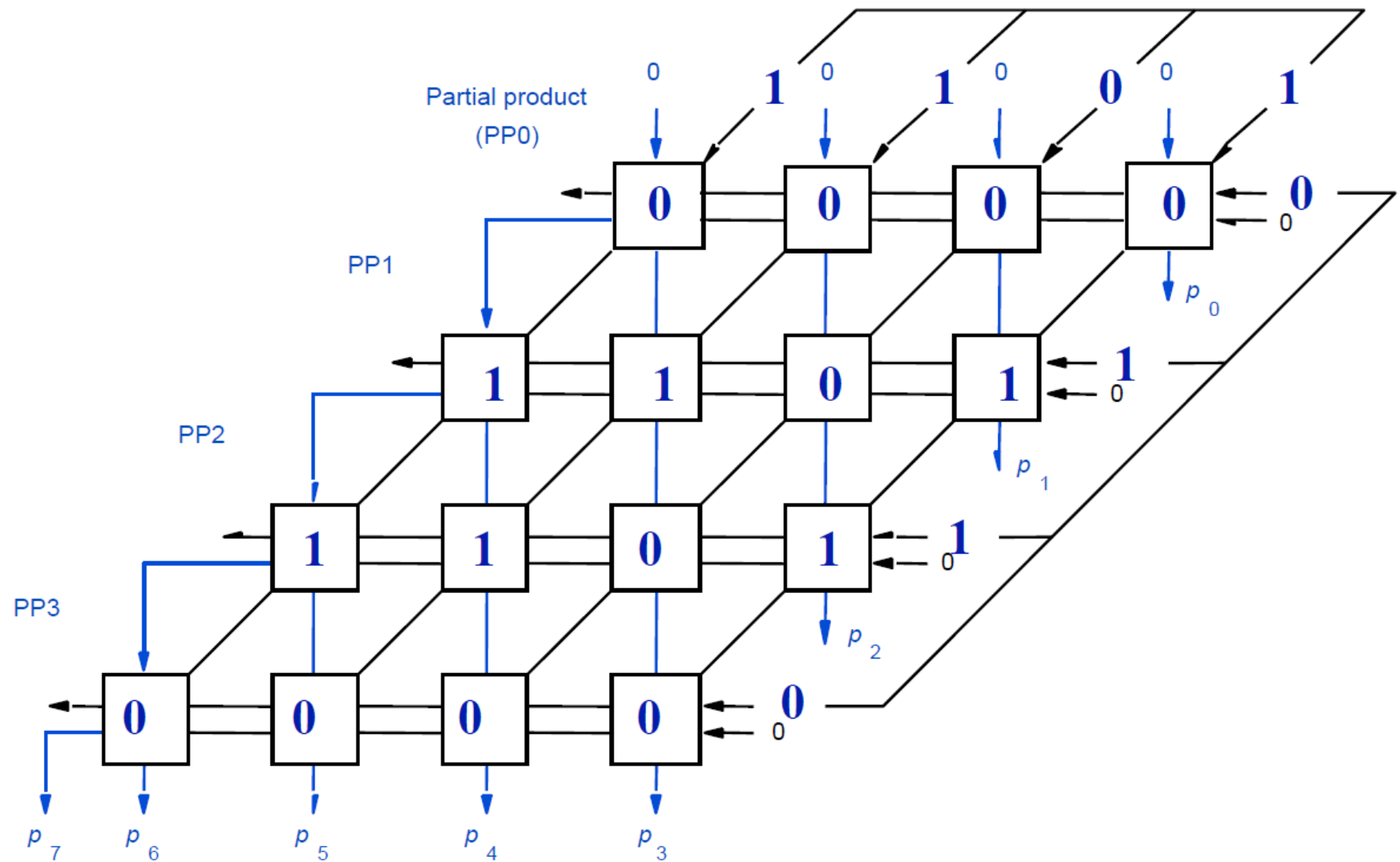


# Multiplier Array Critical Path?

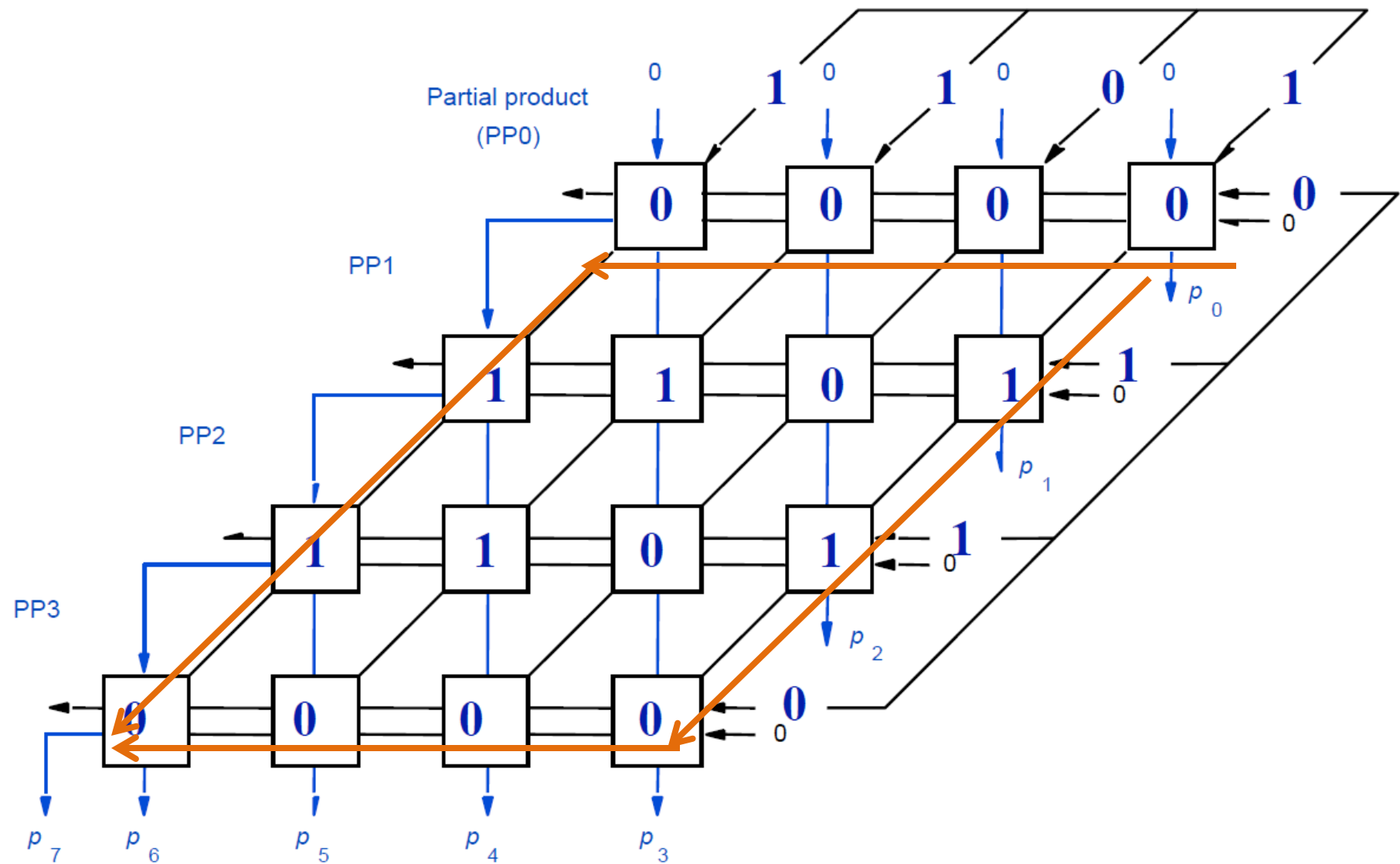



# Multiplier Array Critical Path

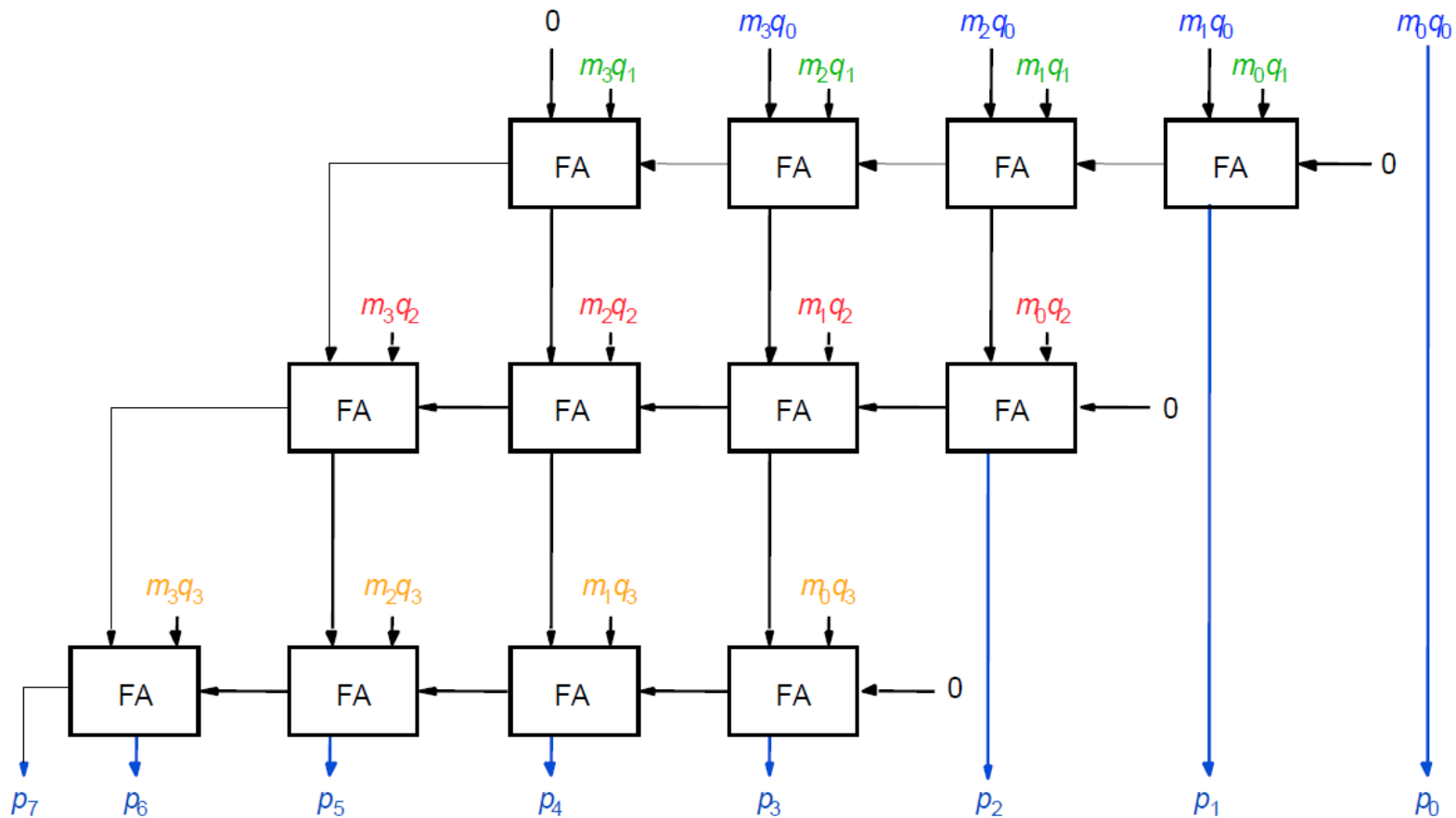

- $A = 0101 (5)$
- $B = 0110 (6)$
- $C = 0011 (3)$
- $A + B + C = 1110 (14)$

# Carry Save Adder: A + B

0 1 0 1

+ 0 1 1 0

---

0 0 1 1

SUM

0 1 0 0

CARRY

No need to propagate Carry

# Redundant Representation

- Represent a number with two bits per digit
- (Sum, Carry)

—(1,0)(1,0)(1,0)(0,0)

—1 1 1 0

- How about this:

—(1,0)(0,0)(1,0)(0,1)?

—1100

# Carry Save Adder: $(A+B) + C$

SUM 0 0 1 1

$A + B$

CARRY 0 1 0 0

0 0 1 1

$C$

---


1 0 0 0

Which number is this?

0 0 1 1


1110

# Carry Save Adder Multiplier Array

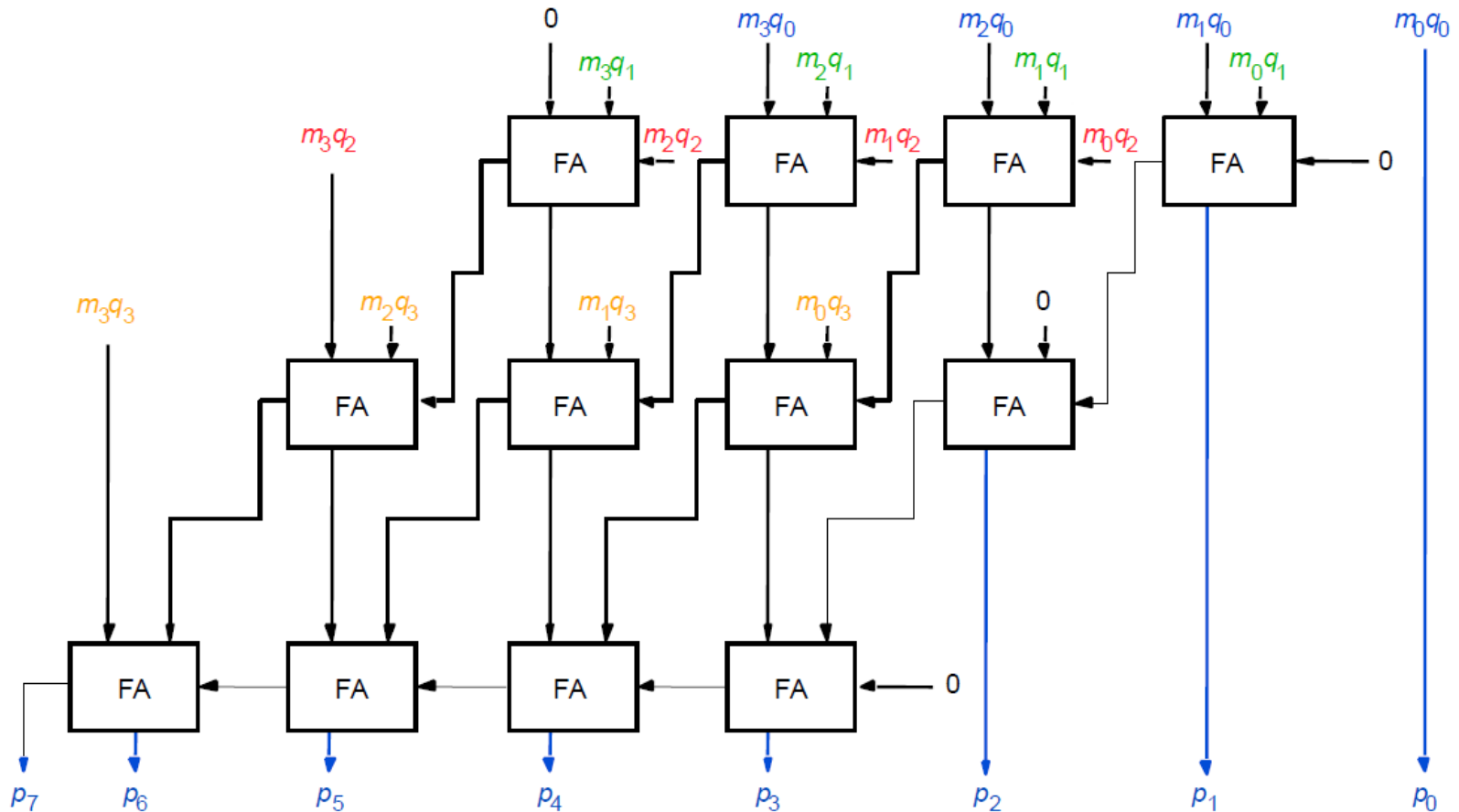
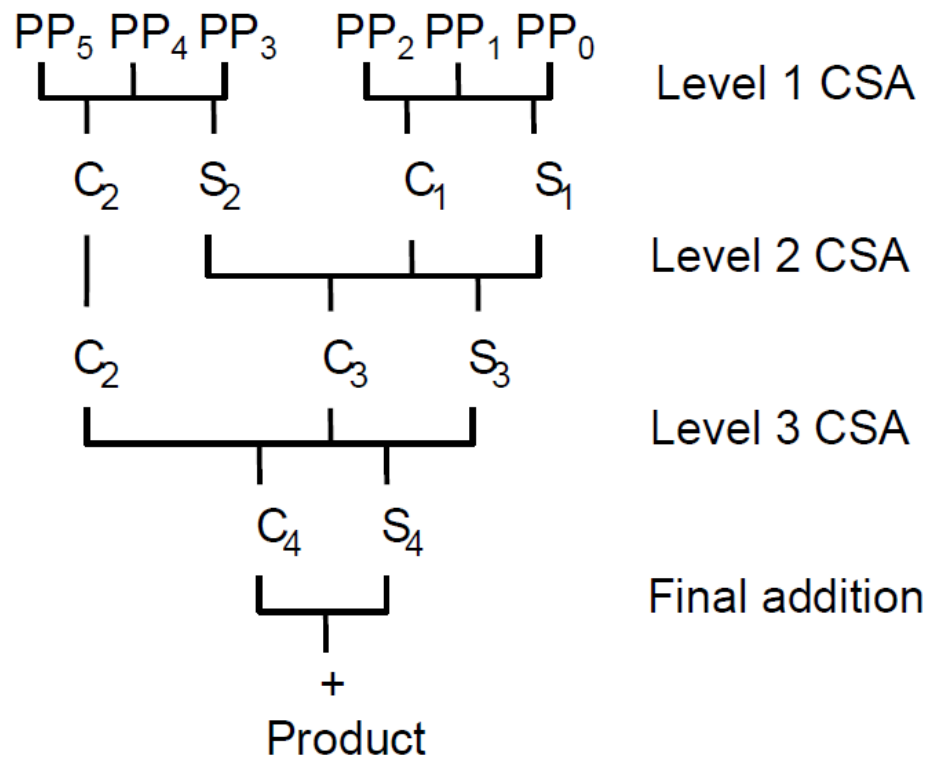
# Wallace Tree

- Addition done hierarchically
  - Groups of 3 partial products added in parallel
  - Produce (sum, carry)
  - (sum, carry) + another output



# Signed Number Multiplication

**1101 ( -3 ) Mand**

**0101 ( 5 ) Mier**

---

**1111101**

**000000**

**11101**

**0000**

---

**11110001 ( -15 )**



# Signed Number Multiplication

111001 ( -7 ) Mand

001110 ( 14 ) Mier

---

000000000000

111111001

11111101

1111101

---

11110011110 ( -98 )

# And now for something different

- Recall:
  - $-A \times (B + C) = A \times B + A \times C$
- $14 = 16 - 2$
- $001110 = 010000 - 000010$

001110

010000

000010

# Signed Number Multiplication

111001 ( -7 ) Mand

0<sup>+</sup>1001<sup>-</sup>0 ( 14 ) Mier

---

000000000000

0000000111

Inverse of -7

0000000000

00000000

Skip these and do a shift by 2

1111001

**Booth's Multiplication**

11110011110 ( -98 )

# Booth Encoding

0011100001111110000000

0<sup>+</sup>100<sup>-</sup>1000<sup>+</sup>1000000<sup>-</sup>10000000

000111111111000011110

00<sup>+</sup>1000000000<sup>-</sup>1000<sup>+</sup>1000<sup>-</sup>10

**01010101010101010**

**+1 -1 +1 -1 +1 -1 +1 -1 +1 -1 +1 -1 +1 -1 +1 -1 +1 -1**

# Booth Encoding Generation


A simple table can be used to generate the booth encoding. As bits in the multiplier are shifted right do:

- Each time there is a transition from a 0 to a 1, the multiplicand is added
- Each time there is a transition from 1 to 0 the inverse of the multiplicand is added
- Otherwise do nothing

Multiplier		Action at position $i$
Bit $i$	Bit $i-1$	
0	0	$0 \times M$
0	1	$1 \times M$
1	0	$-1 \times M$
1	1	$0 \times M$


# 2-bit Booth Recoding

- 0 1 1 0 0 0 0 1 1

 

# 2-bit Booth Recoding

- 1 0 1 1 1 (-9)

 

# Bit-Pair Booth Recoding Example

Example: Multiply 11001 (-7) \* 10111 (-9)

1 1 0 1 1 1 0

-1 +2 -1

Doing the multiplication:

1 1 0 0 1 (-7)

-1 +2 -1 (-9)

---

0 0 0 0 0 0 0 1 1 1

1 1 1 1 0 0 1 0

0 0 0 1 1 1

---

0 0 0 0 1 1 1 1 1 1 (63)

Bit-pair recoding results in fewer additions

- Multiplier arrays will benefit from this as well



# Generating the bit-pair Recording

Multiplier		Next bit in Multiplier ( $i-1$ )	Action at position $i$
$i+1$	$i$		
0	0	0	0xM
0	0	1	1xM
0	1	0	1xM
0	1	1	2xM
1	0	0	-2xM
1	0	1	-1xM
1	1	0	-1xM
1	1	1	0xM

# Division

Division in binary follows the same process as long division by hand:

1. Find the smallest number of digits from the dividend that will be greater than the divisor. For every digit that needs to be taken from the dividend, put a 0 in the quotient.
2. When the portion of the dividend is large enough, add a 1 in to the quotient and subtract the divisor.
3. Repeat until no digits in the dividend are left.


The diagram illustrates the binary long division process. It shows the divisor 1000, the dividend 1001010, and the resulting quotient 1001 with a remainder of 10. Arrows indicate the alignment of the divisor with the dividend and the final remainder.

$$\begin{array}{r} \text{Quotient} \\ \phantom{0}1001 \\ \hline 1000 \overline{) 1001010} \\ \phantom{0} \underline{-1000} \phantom{0} \\ \phantom{00}10 \\ \phantom{00} \phantom{0} \underline{101} \\ \phantom{000}1010 \\ \phantom{000} \underline{-1000} \\ \phantom{0000}10 \\ \text{Remainder} \end{array}$$

Labels in the diagram:

- Quotient**: Points to the result 1001.
- Divisor**: Points to the number 1000.
- Dividend**: Points to the number 1001010.
- Remainder**: Points to the final result 10.

# Simple Divisor

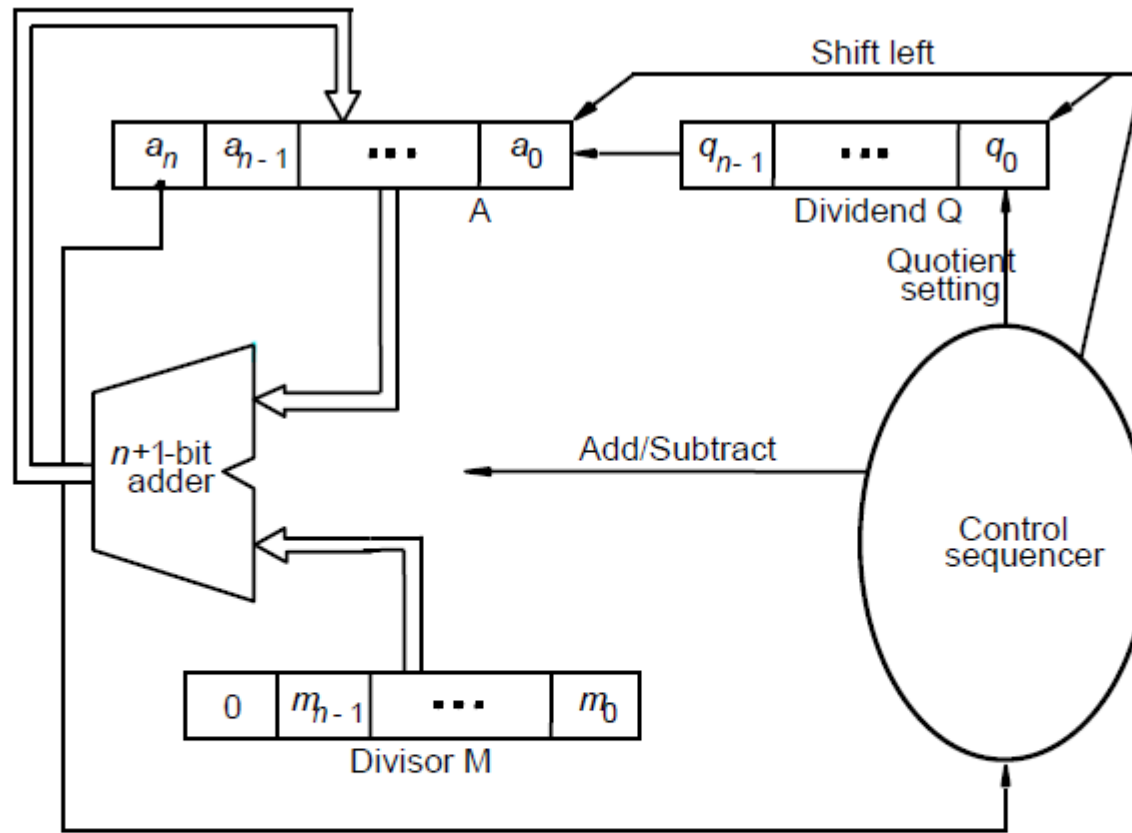

Register A holds the *current remainder* for the division

- The current divisor is compared with the remainder by subtracting it from the remainder and checking the sign of the result.

# Divisor Operation

- Steps for restoring division:
  - 1. Subtract divisor from current remainder
  - 2. Test the new remainder:
    - 1. If positive put a 1 in the quotient
    - 2. If negative put a 0 in the quotient and add the divisor back to the remainder to “restore” it back to its original value.
  - 3. Shift the quotient and dividend left by 1 bit
  - 4. Repeat until all bits in the dividend are consumed.
- **Restoring Division:**
  - Divisor is added back when larger than remainder

# Restoring Division Example

Example:  $1000 \overline{) 1001010}$

Operation	Sign	Register A (Remainder)	Quotient
Shift	0	0100	1010
Subtract	1	1100	10100
Restore	0	0100	10100
Shift	0	1001	0100
Subtract	0	0001	01001
Shift	0	0010	1001
Subtract	1	1010	10010
Restore	0	0010	10010
Shift	0	0101	0010
Subtract	1	1101	00100
Restore	0	0101	00100
Shift	0	1010	0100
Subtract	0	0010	01001

# Non-Restoring Division

- If R is negative we add D to restore value
- Can we avoid this?
- At each step we want to do:  $R - D$
- When negative we do:  $R - D + D$
- Then shift left:  $2 \times R$
- Then subtract D:  $2 \times R - D$
- What if we don't restore:  $R - D$
- Shift:  $2 \times (R - D) = 2 \times R - 2 \times D$
- And we want  $2 \times R - D$
- What to do?  $(2 \times R - 2 \times D) + D$

# Non-Restoring Division Example

Example:  $1000 \overline{)1001010}$

Operation	Sign	Register A (Remainder)	Quotient
Shift	0	0100	1010
Subtract	1	1100	10100
Shift	1	1001	0100
Add/Restore	0	0001	01001
Shift	0	0010	1001
Subtract	1	1010	10010
Shift	1	0101	0010
Add/Restore	1	1101	00100
Shift	1	1010	0100
Add/Restore	0	0010	01001

# SRT Division Pointer

- Sweeney, Robertson, and Tocher Division
- SRT is essentially the same as non-restoring division, but is performed in a higher radix:
  - SRT guesses several digits of the quotient at a time
  - SRT has pre-computed tables that allow it to find the right bits depending on remainder and divisor
  - Like non-restoring, if it overshoots, it makes up for it in following cycles



## On-Chip Networks

Natalie Enright Jerger  
University of Toronto

Li-Shiuan Peh  
Princeton University

*SYNTHESIS LECTURES ON COMPUTER ARCHITECTURE #8*



MORGAN & CLAYPOOL PUBLISHERS